

ECE5001 – Digital System Architecture and Design using HDL

Master of Technology

In

(VLSI DESIGN)

Submitted


to

Dr. Nalluri Purnachand

By

Name:

Roll Number:

 

VIT-AP

UNIVERSITY

LIST OF EXPERIMENTS

S.No	Experiment Name
1	Adders and Subtractors
2	Decoder, Priority Encoder and Mux and De mux
3	N Bit comparator and N bit Adder
4	Flip Flops
5	Universal Counter
6	SRAM Design
7	Universal Shift Registers
8	Floating Point Adder
9	Floating Point Multiplier
10	Boot Multiplier

1. Adders and Subtractors

AIM: Implement all the Adders and Subtractors using FPGA.

Tools: Xilinx Vivado HLx Editions 2018.2 - Z7 FPGA Board (xc7z010clg400-1)

Theory:

1. Half Adder

A Half Adder is a combinational logic circuit that performs the addition of two single-bit binary inputs. It produces:

- Sum (S) , Carry (C)

It does not consider any carry input from a previous stage, hence the name *half* adder.

Logic Equations

- $\text{Sum} = A \oplus B$, $\text{Carry} = A \cdot B$

Truth Table

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

2.Full Adder :

Full Adder is a combinational circuit that adds three inputs and produces two outputs. The first two inputs are A and B and the third input is an input carry as C-IN. The output carry is designated as C-OUT and the normal output is designated as S which is SUM.

The C-OUT is also known as the majority 1's detector, whose output goes high when more than one input is high.

A full adder logic is designed in such a manner that can take eight inputs together to create a byte-wide adder and cascade the carry bit from one adder to another.

Table:-

INPUT			OUTPUT	
A	B	C-IN	Sum	C-OUT
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Half Subtractor:

A half subtractor is a digital logic circuit that performs the binary subtraction of two single-bit binary numbers. It has two inputs, A and B, and two outputs, Difference and Borrow. The Difference output represents the result of subtracting B from A, while the Borrow output indicates whether a borrow is needed when A is smaller than B.

Truth Table:

Inputs		Outputs	
A	B	D (Difference)	B (Borrow)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Full Subtractor:

A Full Subtractor is a combinational circuit used to perform binary subtraction. It has three inputs:

- A (Minuend)
- B (Subtrahend)
- B-IN (Borrow-in from the previous stage)

It produces two outputs:

- Difference (D): The result of the subtraction.
- Borrow-out (B-OUT): Indicates if a borrow is needed for the next stage.

Truth Table of Full Subtractor

Input			Output	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

CODE :-

```
module half_adder_gatelevel (
```

```
    input a, b,
```

```
    output sum, carry
```

```
);
```

```
    xor (sum, a, b);
```

```
    and (carry, a, b);
```

```
endmodule
```

```
module half_adder_dataflow (
```

```
    input a, b,
```

```
    output sum, carry
```

```
);
```

```
assign sum  = a ^ b;
```

```
assign carry = a & b;
```

```
endmodule
```

```
module half_adder_behavioral (
```

```
    input a, b,
```

```
    output reg sum, carry
```

```
);
```

```
always @(*) begin
```

```
    sum  = a ^ b;
```

```
    carry = a & b;
```

```
end
```

```
endmodule
```

```
`timescale 1ns/1ps
```

```
module tb_half_adder();
```

```
    reg a, b;
```

```
    wire sum_g, carry_g;
```

```
    wire sum_d, carry_d;
```

```
    wire sum_b, carry_b;
```

```
// DUT Instances
```

```
half_adder_gatelevel U1 (.a(a), .b(b), .sum(sum_g), .carry(carry_g));
```

```
half_adder_dataflow U2 (.a(a), .b(b), .sum(sum_d), .carry(carry_d));
```

```
half_adder_behavioral U3 (.a(a), .b(b), .sum(sum_b), .carry(carry_b));
```

```
initial begin
```

```
$display("Time | A B | GateLevel(Sum Carry) | Dataflow(Sum Carry) | Behavioral(Sum Carry)");
```

```
$monitor("%4t | %b %b |      %b  %b    |      %b  %b    |      %b  %b",
```

```
    $time, a, b,
```

```
    sum_g, carry_g,
```

```
    sum_d, carry_d,
```

```
    sum_b, carry_b);
```

```
// Apply all input combinations
```

```
a=0; b=0; #10;
```

```
a=0; b=1; #10;
```

```
a=1; b=0; #10;
```

```
a=1; b=1; #10;
```

```
$finish;
```

```
end
```

```
endmodule
```

OUTPUT :


```
# Time | A B | GateLevel(Sum Carry)
# 0 | 0 0 | 0 0
# 10000 | 0 1 | 1 0
# 20000 | 1 0 | 1 0
# 30000 | 1 1 | 0 1
```

/tb/dut/a	-No Data-	0010	1000	0000	0110	0000	1000	0110	0001
/tb/dut/b	-No Data-	0100	0001	1001	0011	1101		0101	0010
/tb/dut/s	-No Data-	0110	1001		0101	1101	0101	0011	
/tb/dut/co	-No Data-	0000			0010	0000	1000	0100	0000

Full Adder :

1. Gate-Level Full Adder

```
module full_adder_gatelevel (
```

```
    input a, b, cin,
```

```
    output sum, cout
```

```
);
```

```
    wire s1, c1, c2;
```

```
    // XOR for sum
```

```
    xor (s1, a, b);
```

```
    xor (sum, s1, cin);
```

```
    // Carry logic
```

```
    and (c1, a, b);
```

```
    and (c2, s1, cin);
```

```
    or (cout, c1, c2);
```

```
endmodule
```

2. Dataflow Full Adder

```
module full_adder_dataflow (  
  
    input a, b, cin,  
  
    output sum, cout  
  
);  
  
    assign sum = a ^ b ^ cin;  
  
    assign cout = (a & b) | (b & cin) | (a & cin);  
  
endmodule
```

3. Behavioral Full Adder

```
module full_adder_behavioral (  
  
    input a, b, cin,  
  
    output reg sum, cout  
  
);  
  
    always @(*) begin  
  
        {cout, sum} = a + b + cin;  
  
    end  
  
endmodule
```

4. Parameterized + Generate Full Adder

This version creates **N-bit Full Adder** using **1-bit full adders**.

```
module full_adder_param #(  
  
    parameter N = 4 // default 4-bit adder
```

```

)(

    input  [N-1:0] a, b,

    input      cin,

    output [N-1:0] sum,

    output      cout

);

wire [N:0] carry;

assign carry[0] = cin;

genvar i;

generate

    for (i = 0; i < N; i = i + 1) begin : FA_LOOP

        full_adder_dataflow FA (

            .a(a[i]), .b(b[i]), .cin(carry[i]),

            .sum(sum[i]), .cout(carry[i+1])

        );

    end

endgenerate

assign cout = carry[N];

endmodule

```

Common Testbench for All Models

```
`timescale 1ns/1ps
```

```

module tb_full_adder;

    reg a, b, cin;

    wire sum_gate, cout_gate;

    wire sum_data, cout_data;

    wire sum_behav, cout_behav;

    // DUTs

    full_adder_gatelevel U1 (.a(a), .b(b), .cin(cin), .sum(sum_gate), .cout(cout_gate));

    full_adder_dataflow U2 (.a(a), .b(b), .cin(cin), .sum(sum_data), .cout(cout_data));

    full_adder_behavioral U3 (.a(a), .b(b), .cin(cin), .sum(sum_behav), .cout(cout_behav));

    // Parameterized 4-bit example

    reg [3:0] A4, B4;

    reg CIN4;

    wire [3:0] SUM4;

    wire COUT4;

    full_adder_param #(.N(4)) U4 (

        .a(A4), .b(B4), .cin(CIN4), .sum(SUM4), .cout(COUT4)

    );

    initial begin

        $display("Full Adder Testbench\n");

        $monitor("T=%0t | A=%b B=%b Cin=%b || Gate: S=%b Cout=%b | Data: S=%b Cout=%b | Behav: S=%b Cout=%b",

            $time, a, b, cin,

```

```

        sum_gate, cout_gate,

        sum_data, cout_data,

        sum_behav, cout_behav);

// 1-bit test

a=0; b=0; cin=0; #10;

a=0; b=1; cin=0; #10;

a=1; b=0; cin=0; #10;

a=1; b=1; cin=0; #10;

a=0; b=0; cin=1; #10;

a=0; b=1; cin=1; #10;

a=1; b=0; cin=1; #10;

a=1; b=1; cin=1; #10;

// 4-bit param test

A4=4'b1010; B4=4'b0111; CIN4=0; #10;

$display("4-bit Param FA: A=%b B=%b CIN=%b -> SUM=%b COUT=%b", A4, B4, CIN4,
SUM4, COUT4);

A4=4'b1111; B4=4'b0001; CIN4=1; #10;

$display("4-bit Param FA: A=%b B=%b CIN=%b -> SUM=%b COUT=%b", A4, B4, CIN4,
SUM4, COUT4);


$finish;

end


endmodule

```

Output (Half Adder) :-

 

Output (Full Adder):-

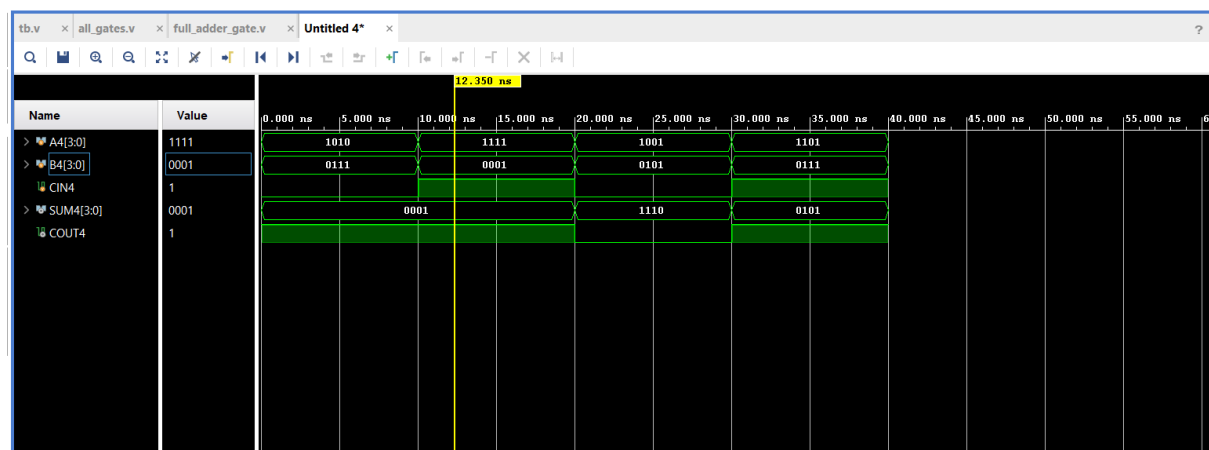

Half Subtractor :-

1. Gate-Level Half Subtractor

```
module half_subtractor_gatelevel (
```

```
    input a, b,
```

```
    output diff, borrow
```

```
);
```

```
    xor (diff, a, b); // Difference
```

```
    not (na, a);
```

```
    and (borrow, na, b); // Borrow = ~a & b
```

```
endmodule
```

2. Dataflow Half Subtractor

```
module half_subtractor_dataflow (
```

```
    input a, b,
```

```
    output diff, borrow
```

```
);
```

```
    assign diff = a ^ b;
```

```
    assign borrow = (~a) & b;
```

```
endmodule
```

3. Behavioral Half Subtractor

```
module half_subtractor_behavioral (
```

```
    input a, b,
```

```
    output reg diff, borrow
```

```
);
```

```
    always @(*) begin
```

```
        diff = a ^ b;
```

```
        borrow = (~a) & b;
```

```
    end
```

```
endmodule
```

4. Parameterized + Generate Half Subtractor

Here we extend to **N-bit Half Subtractor** using **1-bit half subtractors**.

```

module half_subtractor_param #(

    parameter N = 4

)(

    input  [N-1:0] a, b,

    output [N-1:0] diff, borrow

);

    genvar i;

    generate

        for (i = 0; i < N; i = i + 1) begin : HS_LOOP

            half_subtractor_dataflow HS (

                .a(a[i]), .b(b[i]),

                .diff(diff[i]), .borrow(borrow[i])

            );

        end

    endgenerate

endmodule

```

Test Bench for All Levels :-

```
`timescale 1ns/1ps
```

```
module tb_half_subtractor_gatelevel;
```



```

reg a, b;

wire diff, borrow;

// DUT instance

half_subtractor_gatelevel UUT (

    .a(a), .b(b),

    .diff(diff),

    .borrow(borrow)

);

initial begin

    $display("Gate-Level Half Subtractor");

    $display("Time | A B | DIFF BORROW");

    $monitor("%5t | %b %b | %b  %b", $time, a, b, diff, borrow);

    a=0; b=0; #10;

    a=0; b=1; #10;

    a=1; b=0; #10;

    a=1; b=1; #10;


    $finish;

end

endmodule

```

Output:-

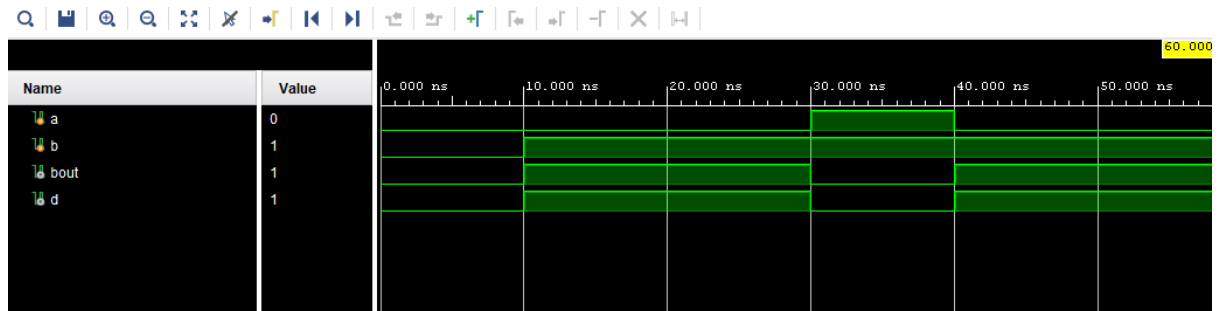

Full Subtractor :-

```

module full_subtractor_gate (
    input a, b, bin,
    output diff, bout );

    wire w1, w2, w3;

    // diff = a ^ b ^ bin
    xor (w1, a, b);
    xor (diff, w1, bin);

    // bout = (~a & b) | (~(a ^ b) & bin)
    and (w2, ~a, b);
    and (w3, ~w1, bin);
    or (bout, w2, w3);
endmodule

module full_subtractor_dataflow (
    input a, b, bin,
    output diff, bout
);

    assign diff = a ^ b ^ bin;

    assign bout = (~a & b) | (~(a ^ b) & bin);

```

```
endmodule
```

```
module full_subtractor_behavioral ( input a, b, bin,
```

```
    output reg diff, bout
```

```
);
```

```
always @(*) begin
```

```
    diff = a ^ b ^ bin;
```

```
    bout = (~a & b) | ~(a ^ b) & bin;
```

```
end
```

```
endmodule
```

Testbench:-

```
`timescale 1ns/1ps;
```

```
module tb_full_subtractor_behavioral;
```

```
    reg a, b, bin;
```

```
    wire diff, bout;
```

```
    full_subtractor_behavioral UUT (.a(a), .b(b), .bin(bin), .diff(diff), .bout(bout));
```

```
    initial begin
```

```
        $display("Behavioral Full Subtractor");
```

```
        $display("time a b bin | diff bout");
```

```
        $monitor("%t %b %b %b | %b %b", $time, a, b, bin, diff, bout);
```

```
        a=0; b=0; bin=0; #10;
```

```
        a=0; b=0; bin=1; #10;
```

```
        a=0; b=1; bin=0; #10;
```

```
        a=0; b=1; bin=1; #10;
```

```
        a=1; b=0; bin=0; #10;
```

a=1; b=0; bin=1; #10;

a=1; b=1; bin=0; #10;

a=1; b=1; bin=1; #10;

\$finish;


end

endmodule

Results:-

Behavioral Full Subtractor

time	a	b	bin		diff	bout
	0	0	0		0	0
10000	0	0	1		1	1
20000	0	1	0		1	1
30000	0	1	1		0	1
40000	1	0	0		1	0
50000	1	0	1		0	0
60000	1	1	0		0	0
70000	1	1	1		1	1

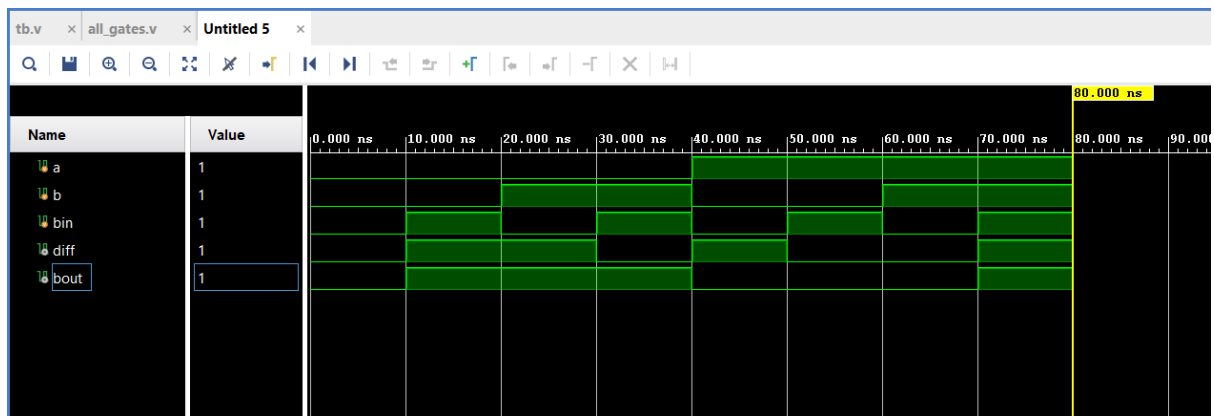

2. Decoder, Priority Encoder and Mux and De-Mux

AIM: Implement all the Decoder, Priority Encoder and Multiplexer, De-Mux using FPGA.

Tools: Xilinx Vivado HLx Editions 2018.2 - Z7 FPGA Board (xc7z010clg400-1)


Theory:

1. Decoder :

The combinational circuit that change the binary information into $2N$ output lines is known as Decoders. The binary information is passed in the form of N input lines. The output lines define the $2N$ -bit code for the binary information. In simple words, the Decoder performs the reverse operation of the Encoder. At a time, only one input line is activated for simplicity. The produced $2N$ -bit output code is equivalent to the binary information.

Truth Table:


Block Diagram:

 

Enable	INPUTS		OUTPUTS			
E	A ₁	A ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

 2. Priority Encoder :

An Encoder is a combinational circuit that performs the reverse operation of Decoder. It has maximum of $2n$ input lines and ' n ' output lines. It will produce a binary code equivalent to the input, which is active High. Therefore, the encoder encodes $2n$ input lines with ' n ' bits. It is optional to represent the enable signal in encoders.




Inputs				Outputs		
I ₀	I ₁	I ₂	I ₃	X	Y	IST
1	x	x	x	0	0	1
0	1	x	x	0	1	1
0	0	1	x	1	0	1
0	0	0	1	1	1	1
0	0	0	0	x	x	0

 3. Multiplexer:

A multiplexer is a combinational circuit that has $2n$ input lines and a single output line. Simply, the multiplexer is a multi-input and single-output combinational circuit. The binary information is received from the input lines and directed to the output line. On the basis of the values of the selection lines, one of these data inputs will be connected to the output.

In the 8 to 1 multiplexer, there are total eight inputs, i.e., A₀, A₁, A₂, A₃, A₄, A₅, A₆, and A₇, 3 selection lines, i.e., S₀, S₁ and S₂ and single output, i.e., Y. On the basis of the combination of inputs that are present at the selection lines S₀, S₁, and S₂, one of these 8 inputs are connected to the output. The block diagram and the truth table of the 8×1 multiplexer are given below.




Truth Table:

INPUTS			Output
S ₂	S ₁	S ₀	Y
0	0	0	A ₀
0	0	1	A ₁
0	1	0	A ₂
0	1	1	A ₃
1	0	0	A ₄
1	0	1	A ₅
1	1	0	A ₆
1	1	1	A ₇

Demultiplexer :-

A De-mux (Demultiplexer)is a digital circuit that takes a single input signal and routes it to one of several output lines, acting as a data distributor or a single-to-many switch, the reverse of a multiplexer (MUX), using control/select lines to choose the destination output. De-muxes are vital in communications and computing for directing data from one source to multiple destinations, like converting serial data to parallel or routing signals in networks .

 

Truth Table: -

Selection Inputs			Outputs							
S2	S1	S0	Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	0	0	0	I
0	0	1	0	0	0	0	0	0	I	0
0	1	0	0	0	0	0	0	I	0	0
0	1	1	0	0	0	0	I	0	0	0
1	0	0	0	0	0	I	0	0	0	0
1	0	1	0	0	I	0	0	0	0	0
1	1	0	0	I	0	0	0	0	0	0
1	1	1	I	0	0	0	0	0	0	0

Code: -

```
module decoder3x8(
    input A, B, C,
    output Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7
);
    wire Abar, Bbar, Cbar;

    // Generate complements
    not (Abar, A);
    not (Bbar, B);
    not (Cbar, C);

    // AND gates for each output line
    and (Y0, Abar, Bbar, Cbar); // 000
    and (Y1, Abar, Bbar, C);    // 001
    and (Y2, Abar, B, Cbar);    // 010
    and (Y3, Abar, B, C);       // 011
    and (Y4, A, Bbar, Cbar);    // 100
    and (Y5, A, Bbar, C);       // 101
    and (Y6, A, B, Cbar);       // 110
    and (Y7, A, B, C);          // 111

endmodule
```

Data Flow :-

```
module tb_oct_to_bin_dataflow;

    reg [7:0] d;

    wire [2:0] bin;

    // Instantiate the gate-level encoder

    oct_to_bin_dataflow uut (.d(d), .bin(bin));

endmodule
```



```
// Monitor signals continuously
```

```
initial begin
```

```
    $monitor("Time=%0t | Input d=%b | Binary Output=%b", $time, d, bin);
```

```
end
```

```
// Apply test vectors
```

```
initial begin
```

```
    $display("Octal-to-Binary Data flow Level Test");
```

```
    d = 8'b00000001; #10;
```

```
    d = 8'b00000010; #10;
```

```
    d = 8'b00000100; #10;
```

```
    d = 8'b00001000; #10;
```

```
    d = 8'b00010000; #10;
```

```
    d = 8'b00100000; #10;
```

```
    d = 8'b01000000; #10;
```

```
    d = 8'b10000000; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

Behavioural:

```
module oct_to_bin_beh(
```

```
    input [7:0] d,
```

```
    output reg [2:0] bin
```

);

always @(*) begin

case (1'b1)

d[0]: bin = 3'd0;

d[1]: bin = 3'd1;

d[2]: bin = 3'd2;

d[3]: bin = 3'd3;

d[4]: bin = 3'd4;

d[5]: bin = 3'd5;

d[6]: bin = 3'd6;

d[7]: bin = 3'd7;

default: bin = 3'd0;

endcase

end

endmodule

module tb_oct_to_bin_beh;

reg [7:0] d;

wire [2:0] bin;

oct_to_bin_beh uut (.d(d), .bin(bin));

initial begin

\$display("Octal-to-Binary Behavioral Test");

d = 8'b00000001; #10;

d = 8'b00000010; #10;

d = 8'b00000100; #10;

d = 8'b00001000; #10;

```

        d = 8'b10000000; #10;

        $finish;

    end


    initial begin

        #10 $monitor("Time=%0t | Input d=%b | Binary Output=%b", $time, d, bin);

    end

endmodule

```

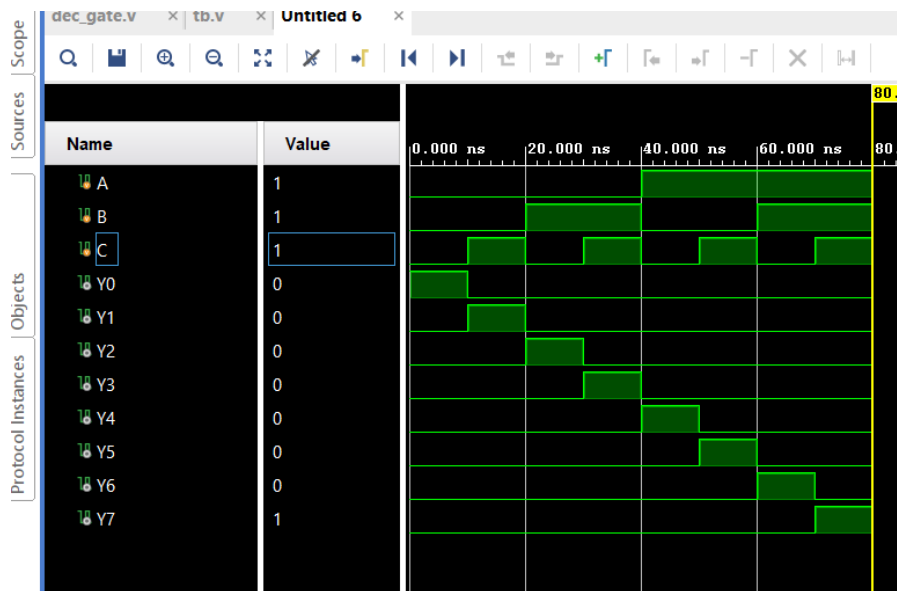

Priority Encoder :-

```

module enc_8X3(

    input [7:0] i,

    output reg [2:0] y);

    always @ (*) begin

        casex(i)

            8'b 1xxxxxxx: y = 3'b 111;

```

```
8'b x1xxxxxx: y = 3'b 110;
```

```
8'b xx1xxxxx: y = 3'b 101;
```

```
8'b xxx1xxxx: y = 3'b 100;
```

```
8'b xxxx1xxx: y = 3'b 011;
```

```
8'b xxxxx1xx: y = 3'b 010;
```

```
8'b xxxxxx1x: y = 3'b 001;
```

```
8'b xxxxxxx1: y = 3'b 000;
```

```
default: begin end
```

```
endcase
```

```
end
```

```
endmodule
```

```
module tb_priority_encoder_8x3_gate;
```

```
    reg [7:0] i_tb;
```

```
    wire [2:0] y_tb;
```

```
    wire en_out_tb;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    priority_encoder_8x3_gate dut (
```

```
        .i(i_tb),
```

```
        .y(y_tb),
```

```
        .en_out(en_out_tb)
```

```
    );
```

```
initial begin
```

```
    // Initialize inputs
```

```
    i_tb = 8'b00000000;
```

```
    #10;
```

```
    // Test cases for priority encoder
```

```
    i_tb = 8'b00000001; // i[0] active
```

```
    #10;
```

```
    i_tb = 8'b00000010; // i[1] active
```

```
    #10;
```

```
    i_tb = 8'b00000100; // i[2] active
```

```
    #10;
```

```
    i_tb = 8'b00001000; // i[3] active
```

```
    #10;
```

```
    i_tb = 8'b00010000; // i[4] active
```

```
    #10;
```

```
    i_tb = 8'b00100000; // i[5] active
```

```
    #10;
```

```
    i_tb = 8'b01000000; // i[6] active
```

```
    #10;
```

```
    i_tb = 8'b10000000; // i[7] active
```

```
    #10;
```

```

// Test cases with multiple inputs active (priority should be observed)

i_tb = 8'b00000011; // i[1] has priority over i[0]

#10;

i_tb = 8'b00100001; // i[5] has priority over i[0]

#10;

i_tb = 8'b11111111; // i[7] has highest priority

#10;

i_tb = 8'b00000000; // No input active

#10;

$finish; // End simulation

end

initial begin


    $monitor("Time=%0t, Input i=%b, Output y=%b, Enable_out=%b", $time, i_tb, y_tb,
en_out_tb);

end

endmodule

```

Output:

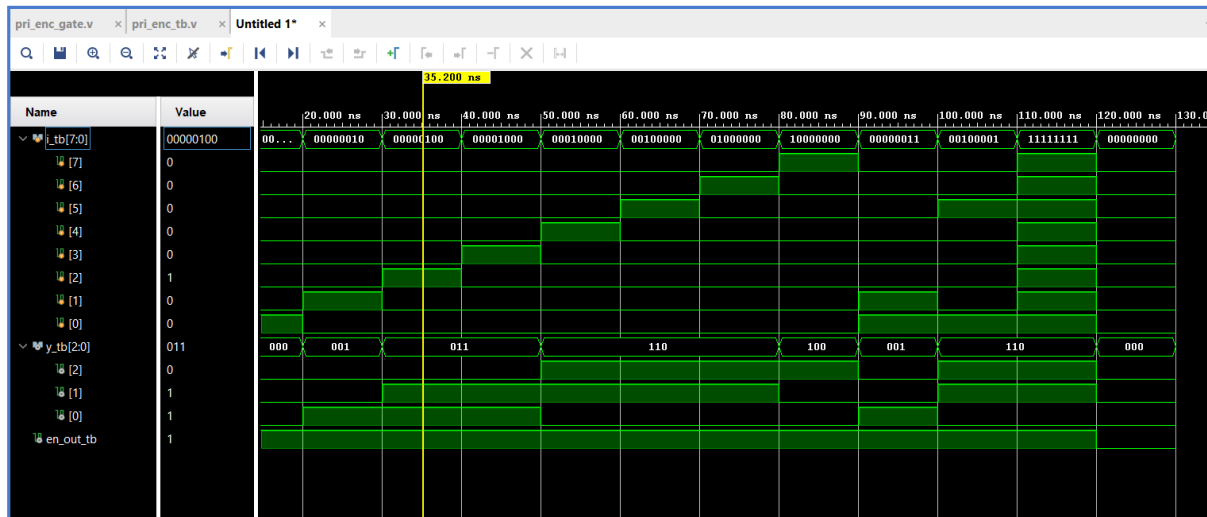

Multiplexer (8 X 1) :-

```
module mux8to1_behavioral (    input  d0, d1, d2, d3, d4, d5, d6, d7,
```

```
    input  [2:0] sel, output reg y );
```

```
always @(*) begin
```

```
    case (sel)
```

```
        3'b000: y = d0;
```

```
        3'b001: y = d1;
```

```
        3'b010: y = d2;
```

```
        3'b011: y = d3;
```

```
        3'b100: y = d4;
```

```
        3'b101: y = d5;
```

```
        3'b110: y = d6;
```

```
        3'b111: y = d7;
```

```
        default: y = 0;
```

```
    endcase
```

end

endmodule

Test Bench:-

```
module tb_decoder3x8;
```

```
    reg A, B, C;
```

```
    wire Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7;
```

```
    decoder3x8 uut (A, B, C, Y0, Y1, Y2, Y3, Y4, Y5, Y6, Y7);
```

```
    initial begin
```

```
        $monitor("A=%b B=%b C=%b => Y7..Y0=%b%b%b%b%b%b%b%b",
```

```
                A, B, C, Y7, Y6, Y5, Y4, Y3, Y2, Y1, Y0);
```

```
        A=0; B=0; C=0; #10;
```

```
        A=0; B=0; C=1; #10;
```

```
        A=0; B=1; C=0; #10;
```

```
        A=0; B=1; C=1; #10;
```

```
        A=1; B=0; C=0; #10;
```

```
        A=1; B=0; C=1; #10;
```

```
        A=1; B=1; C=0; #10;
```

```
        A=1; B=1; C=1; #10;
```


```
        $stop;
```

```
    end
```

```
endmodule
```


Results and Simulation:
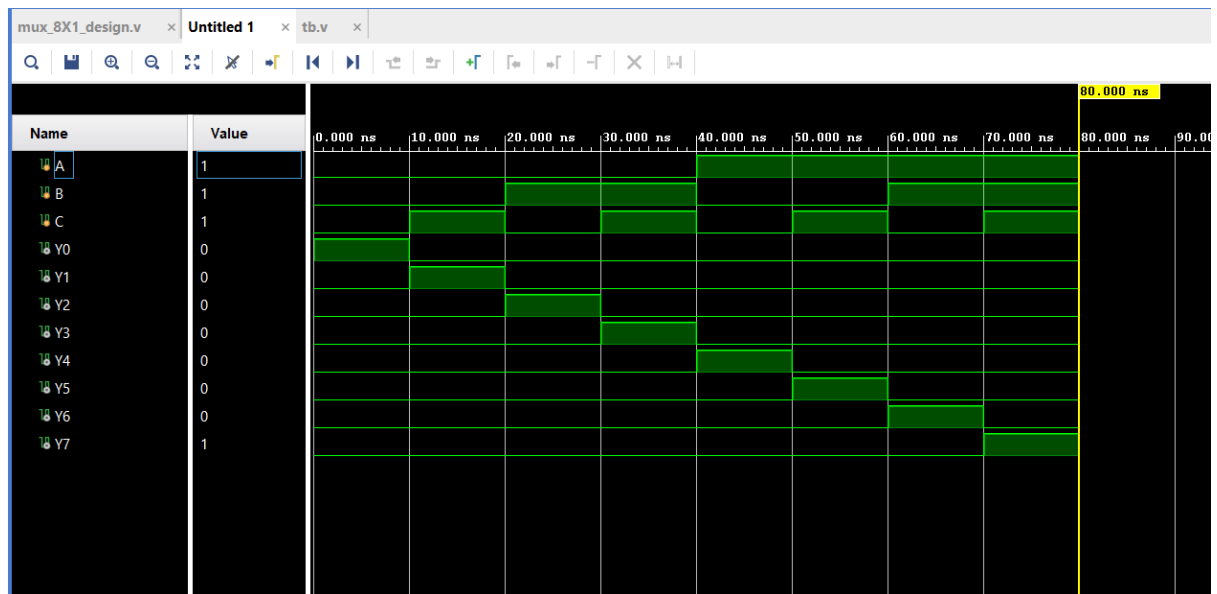
```
# run 1000ns
A=0 B=0 C=0 => Y7..Y0=00000001
A=0 B=0 C=1 => Y7..Y0=00000010
A=0 B=1 C=0 => Y7..Y0=00000100
A=0 B=1 C=1 => Y7..Y0=00001000
A=1 B=0 C=0 => Y7..Y0=00010000
A=1 B=0 C=1 => Y7..Y0=00100000
A=1 B=1 C=0 => Y7..Y0=01000000
A=1 B=1 C=1 => Y7..Y0=10000000
```



De-Multiplexer :-

```
module demux1x8_behav (
```

```
    input d,
```

```
    input [2:0] sel,
```

```
    output reg [7:0] y
```

```
);
```

```
always @(*) begin
```

```
    y = 8'b00000000; // default
```

```
    if (d) begin
```

```

    case (sel)

        3'b000: y[0] = 1;

        3'b001: y[1] = 1;

        3'b010: y[2] = 1;

        3'b011: y[3] = 1;

        3'b100: y[4] = 1;

        3'b101: y[5] = 1;

        3'b110: y[6] = 1;

        3'b111: y[7] = 1;

    endcase

end

end

endmodule

```

Testbench:-

```

`timescale 1ns/1ps

module tb_demux1x8_behav;

    reg d;

    reg [2:0] sel;

    wire [7:0] y;

    demux1x8_behav DUT (.d(d), .sel(sel), .y(y));

    initial begin

```

```
$monitor("Time=%0t d=%b sel=%b -> y=%b", $time, d, sel, y);
```

```
d = 0; sel = 3'b000; #10;
```

```
d = 1;
```

```
repeat (8) begin
```

```
    sel = sel + 1; #10;
```

```
end
```


```
d = 0; sel = 3'b110; #10;
```

```
$finish;
```

```
end
```

```
endmodule
```

Results and simulation :-

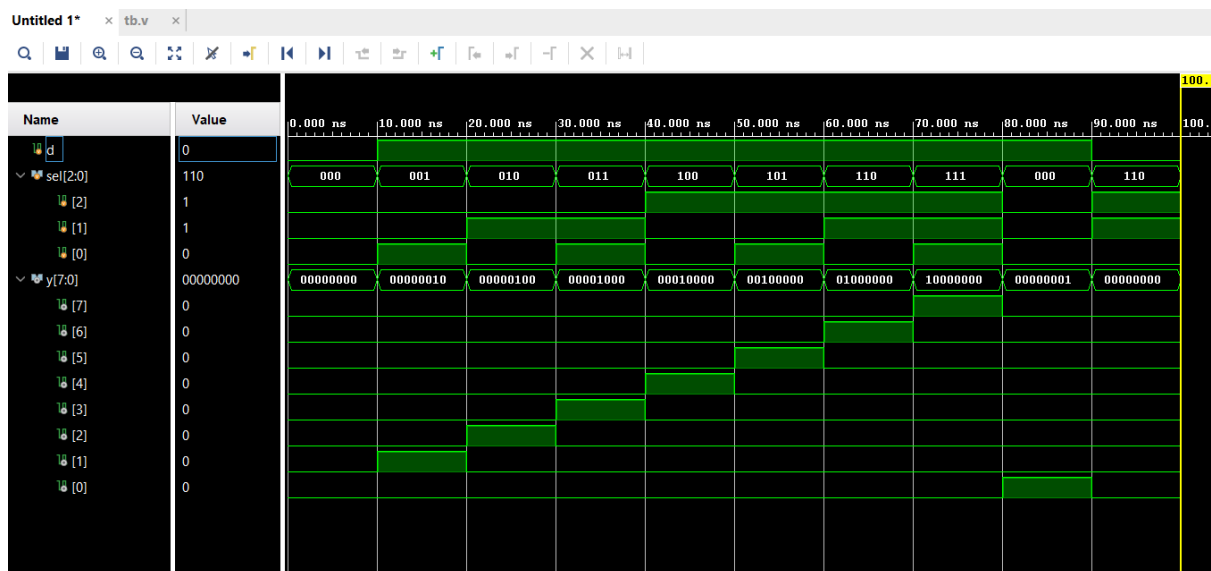

```
Time=0 d=0 sel=000 -> y=00000000
Time=10000 d=1 sel=001 -> y=00000010
Time=20000 d=1 sel=010 -> y=00000100
Time=30000 d=1 sel=011 -> y=00001000
Time=40000 d=1 sel=100 -> y=00010000
Time=50000 d=1 sel=101 -> y=00100000
Time=60000 d=1 sel=110 -> y=01000000
Time=70000 d=1 sel=111 -> y=10000000
Time=80000 d=1 sel=000 -> y=00000001
Time=90000 d=0 sel=110 -> y=00000000
```

3. N Bit Comparator and N Bit Binary Adder


AIM: Implement the N Bit Comparator and N Bit Binary Adder using FPGA.

Tools: Xilinx Vivado HLx Editions 2018.2 - Z7 FPGA Board (xc7z010clg400-1)

Theory:


N-Bit Comparator: -

A digital Comparator is a combinational circuit that compares two digital or binary numbers in order to find out whether one binary number is equal, less than, or greater than the other binary number. We logically design a circuit for which we will have two inputs one for A and the other for B and have three output terminals, one for $A > B$ condition, one for $A = B$ condition, and one for $A < B$ condition.

 

N-Bit Binary Adder:-

 Full adder can add single bit two inputs and extra carry bit generated from its previous stage. To add multiple 'n' bits binary sequence, multiples cascaded full adders can be used which can generate a carry bit and be applied to the next stage full adder as an input till the last stage of full adder. This appears as carry-bit ripples to the next stage, hence it is known as "Ripple carry adder".



4-Bit Ripple Carry Adder

Code :

```
module comp_bh #(parameter N=4)(  
  
    input [N-1:0]a,  
  
    input[N-1:0]b,  
  
    output g,e,l,g_e,l_e  
  
);  
  
assign {g,e,l,g_e,l_e}={ (a>b),(a==b),(a<b),(a>=b),(a<=b)};  
  
endmodule
```

Test Bench:-

```
module comp_tb #(parameter N=4)();  
  
    reg [N-1:0]a;  
  
    reg [N-1:0]b;  
  
    wire g,e,l,g_e,l_e;  
  
    comp_bh DUT(a,b,g,e,l,g_e,l_e);  
  
    initial begin  
  
        $monitor("a=%b,b=%b,g=%b,e=%b,l=%b,g_e=%b,l_e=%b",a,b,g,e,l,g_e,l_e);  
  
        #10;  
  
        repeat(10) begin  
  
            {a,b}=$random();  
  
            #10;
```

end

```
$finish();
```

end

endmodule

Results and Simulations: -

a=xxxx,b=xxxx,g=x,e=x,l=x,g_e=x,l_e=x

a=0010,b=0100,g=0,e=0,l=1,g_e=0,l_e=1

$a=1000, b=0001, g=1, e=0, l=0, g_e=1, l_e=0$

a=0000,b=1001,g=0,e=0,l=1,g_e=0,l_e=1

a=0110,b=0011,g=1,e=0,l=0,g_e=1,l_e=0

a=0000,b=1101,g=0,e=0,l=1,g e=0,l e=1


a=1000,b=1101,g=0,e=0,l=1,g_e=0,l_e=1

a=0110,b=0101,g=1,e=0,l=0,g_e=1,l_e=0

a=0001,b=0010,g=0,e=0,l=1,g_e=0,l_e=1

a=0000,b=0001,g=0,e=0,l=1,g_e=0,l_e=1

a=0000,b=1101,g=0,e=0,l=1,g_e=0,l_e=1

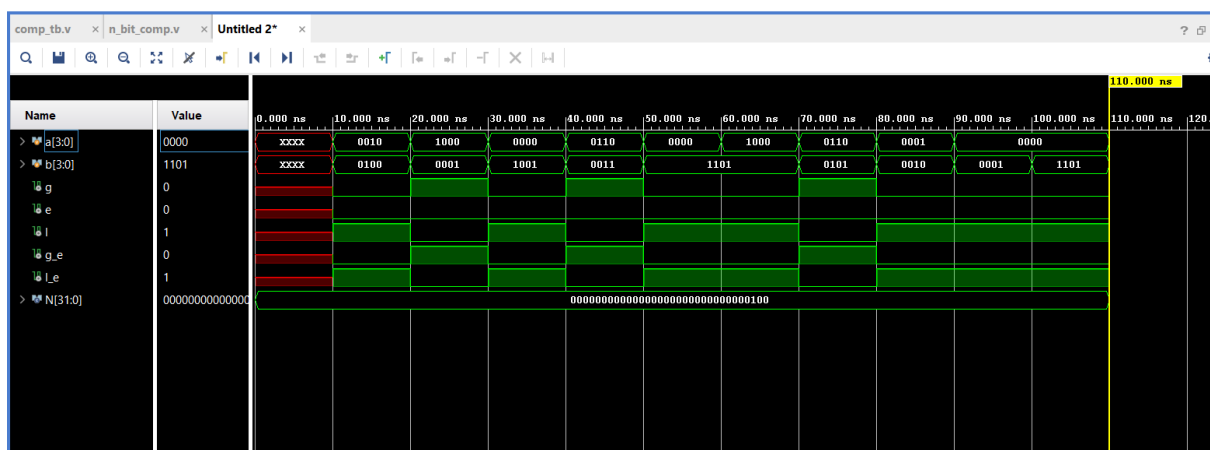

N_Bit Adder :-

```
module n_bit_adder #(parameter N=8)(  
  
    input [N-1:0]b ,  
  
    input [N-1:0]a ,  
  
    input cin,  
  
    output [N-1:0] sum,  
  
    output cy );  
  
    wire [N:0] carry;  
  
    assign carry[0]= cin;  
  
    assign cy = carry[N];  
  
    genvar i;  
  
    generate  
  
        for(i=0;i<N;i=i+1) begin  
  
            full_adder_behavioral NFA(.a(a[i]),.b(b[i]),.cin(carry[i]),.cout(carry[i+1]),.sum(sum[i]) );  
  
        end  
  
    endgenerate  
  
endmodule
```

TestBench :-

```
module n_bit_adder_tb #(parameter N=8);  
  
    reg [N-1:0]a ;  
  
    reg [N-1:0]b ;
```



```
reg cin;
```

```
wire [N-1:0] sum;
```

```
wire cy;
```

```
n_bit_adder dut (a,b,cin,sum,cy);
```

```
initial begin
```

```
$monitor("a=%b b=%b cin=%b sum=%b cy=%b",a,b,cin,sum,cy);
```

```
repeat (10) begin
```

```
    a=$random();
```

```
    b=$random();
```

```
    cin = $random()%2;
```

```
    #10 ;
```


```
end
```

```
    $finish;
```

```
end
```

```
endmodule
```

Results and Simulation :-

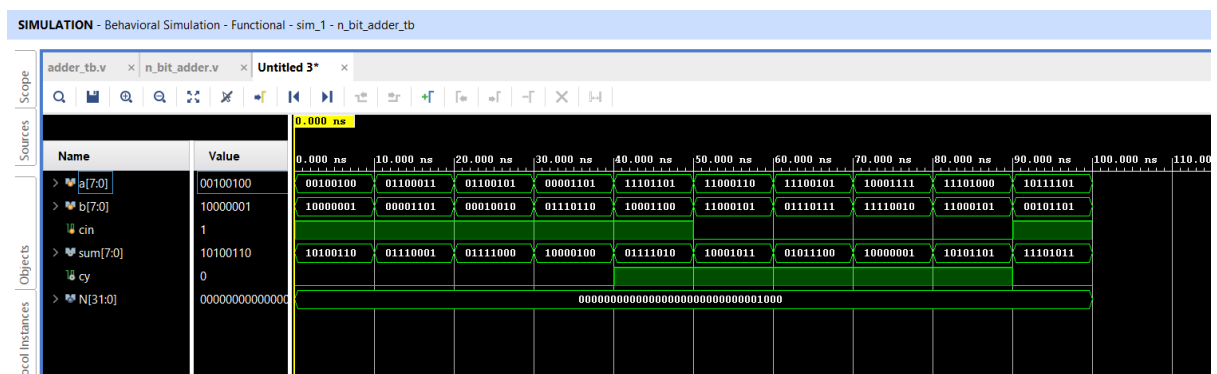

```
a=00100100 b=10000001 cin=1 sum=10100110 cy=0
a=01100011 b=00001101 cin=1 sum=01110001 cy=0
a=01100101 b=00010010 cin=1 sum=01111000 cy=0
a=00001101 b=01110110 cin=1 sum=10000100 cy=0
a=11101101 b=10001100 cin=1 sum=01111010 cy=1
a=11000110 b=11000101 cin=0 sum=10001011 cy=1
a=11100101 b=01110111 cin=0 sum=01011100 cy=1
a=10001111 b=11110010 cin=0 sum=10000001 cy=1
a=11101000 b=11000101 cin=0 sum=10101101 cy=1
a=10111101 b=00101101 cin=1 sum=11101011 cy=0
```

4. FlipFlops


AIM: Implement all the FLIPFLOPS.

Tools: Xilinx Vivado HLx Editions 2018.2 - Z7 FPGA Board (xc7z010clg400-1)

Theory:

SR FLIPFLOP:

 It is a Flip Flop with two inputs, one is S and other is R. S here stands for Set and R here stands for Reset. Set basically indicates set the flip flop which means output 1 and reset indicates resetting the flip flop which means output 0. Here clock pulse is supplied to operate this flip flop, hence it is clocked flip flop.




S	R	Q_{n+1}
0	0	Q_n (No Change)
0	1	0
1	0	1
1	1	x

JK FLIPFLOP:

- The JK flip flop is used to remove the drawback of the S-R flip flop, i.e., undefined states.
- The JK flip flop is formed by doing modification in the SR flip flop.
- When S and R input is set to true, the SR flip flop gives an inaccurate result. But in the case of JK flip flop, it gives the correct output.
- When the input J and K are different then the output Q takes the value of J at the next clock edge.
- When J and K both are low then NO change occurs at the output.

 
- If both J and K are high, then at the clock edge, the output will toggle from one state to the other.



J	K	Q_{n+1}
0	0	Q_n (No Change)
0	1	0
1	0	1
1	1	$\overline{Q_n}$ (Toggles)

T-Flip Flop: -

 T flip flop or to be precise is known as Toggle Flip Flop because it can able to toggle its output depending upon on the input. There stands for Toggle. Toggle basically indicates that the bit will be flipped i.e., either from 1 to 0 or from 0 to 1. Here, a clock pulse is supplied to operate this flop, hence it is a clocked flip-flop.



Truth Table


T	Q_{n+1}
0	Q_n (No Change)
1	$\overline{Q_n}$ (Toggles)

D-Flip Flop:-

D flip flop is an electronic device that is known as “delay flip flop” or “data flip flop” which is used to store single bit of data.

The D flip flop has two inputs, data and clock input which controls the flip flop. when clock input is high, the data is transferred to the output of the flip flop.

 when the clock input is low, the output of the flip flop is held in its previous state.



D	CLK	\bar{Q}
0	Rising Edge	0
1	Rising Edge	1

Code:-

SR:

```
module sr_flipflop(  
  
    input s,r,rst,clk,  
  
    output reg q,q_bar);  
  
    always @(posedge clk) begin  
  
        if(rst) begin  
  
            q<=0;  
  
            q_bar<=1;  
  
            end  
  
        else begin
```

```
case({s,r})
```

```
2'b00:begin
```

```
    q<=q; q_bar<=q_bar;
```

```
end
```

```
2'b01:begin
```

```
    q<=0; q_bar<=1;
```

```
end
```

```
2'b10:begin
```

```
    q<=1; q_bar<=0;
```

```
end
```

```
2'b11: begin
```

```
end
```

```
default : begin
```

```
end
```

```
endcase
```

```
end
```

```
end
```

```
endmodule
```

Test Bench:

```
module sr_tb();
```

```
reg s,r,rst,clk;
```

```

wire q,q_bar;

sr_flipflop dut(s,r,rst,clk,q,q_bar);

initial clk=0;

always #5 clk=~clk);

initial begin

rst=1;#10; rst=0;#10;

{s,r}=2'b10;#20;

{s,r}=2'b01;#20;

{s,r}=2'b00;#20;


{s,r}=2'b11;#20;

$finish();

end

endmodule

```

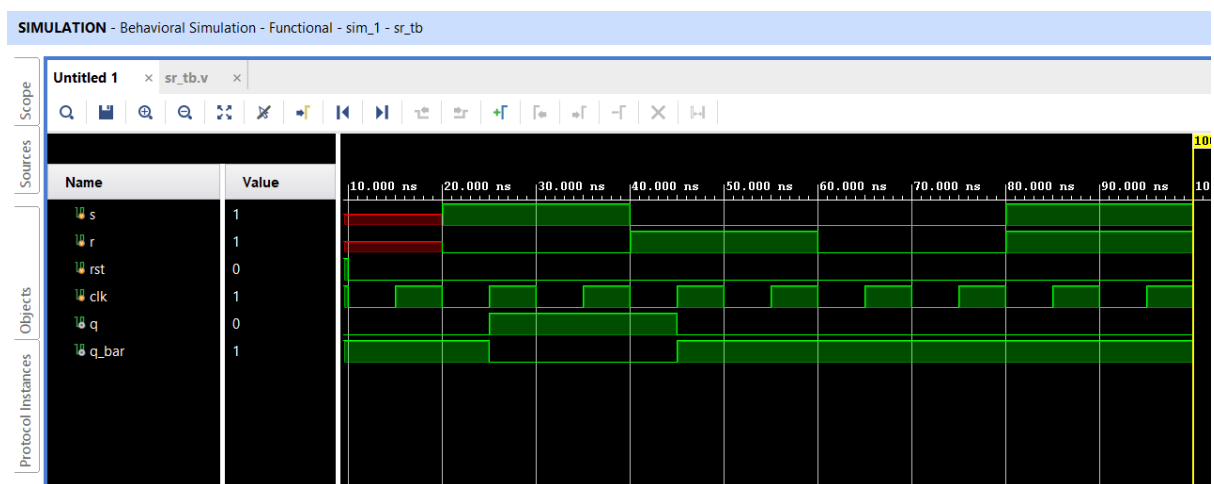

JK FLIPFLOP :-

```
module jk_ff(  
  
    input j,k,rst,clk,  
  
    output reg q,q_bar);  
  
    always @(posedge clk) begin  
  
        if(rst) begin  
  
            q<=1; q_bar<=0;  
  
        end  
  
        else begin  
  
            case({j,k})  
  
                2'b00 : {q,q_bar} <= {q,q_bar};  
  
                2'b01 : {q,q_bar} <= 2'b01;  
  
                2'b10 : {q,q_bar} <= 2'b10;  
  
                2'b11 : {q,q_bar} <= {q_bar,q};  
  
                default: begin end  
  
            endcase  
  
        end  
  
    end  
  
endmodule
```

```
module jk_tb();
```



```
reg j,k,rst,clk;

wire q,q_bar;

jk_ff dut(j,k,rst,clk,q,q_bar);

initial clk=0;

always #5 clk = ~clk;

initial begin

    rst=1;#10;

    rst=0;#10;


    {j,k}=2'b00;#20;

    {j,k}=2'b01;#20;


    {j,k}=2'b10;#20;

    {j,k}=2'b11;#20;

    $finish();

end

endmodule
```

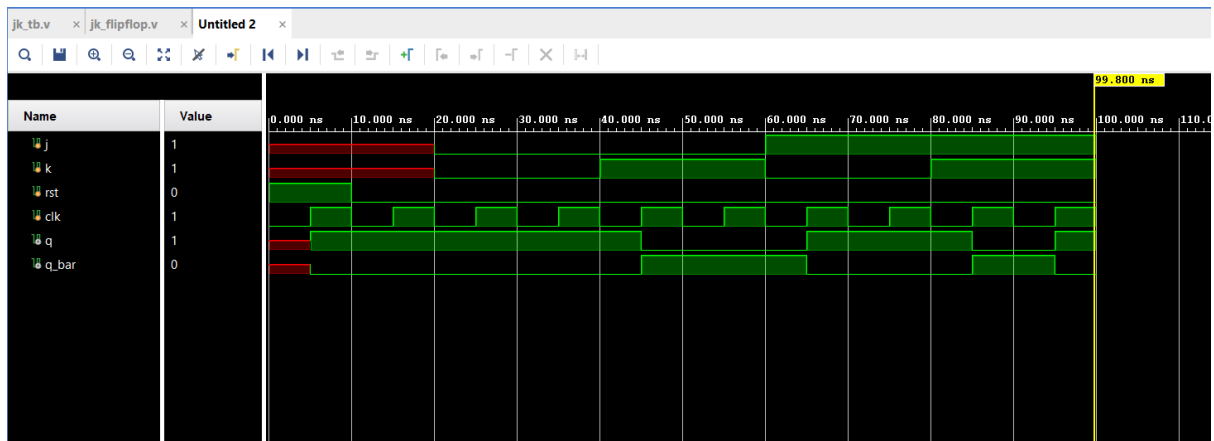

D FLIP FLOP :-

```
module dff (
```

```
    input clk,
```

```
    input reset,
```

```
    input d,
```

```
    output reg q,
```

```
    output reg qbar
```

```
);
```

```
always @(posedge clk or posedge reset) begin
```

```
    if (reset) begin
```

```
        q <= 1'bX;
```

```
        qbar <= 1'bx;
```

```
    end
```

```
    else begin
```

```
        q <= d;
```

```

        qbar <= ~d;

    end

end

endmodule


module d_tb;

reg clk, reset, d;

wire q , qbar;

dff dut ( .clk(clk), .reset(reset), .d(d),.q(q),.qbar(qbar));


initial begin

    clk <= 1'b0;

    reset <= 1'b1;

    d <= 1'b0;

    #10 reset <= 1'b0;

    #10 d <= 1'b1;

    #10 d <= 1'b0;

    #10 d <= 1'b1;

    #10 $finish;

end

always #5 clk <= ~clk;


```

```
initial begin
```

```
$monitor("clk = %b, reset = %b, d = %b, q = %b , qbar =%b", clk, reset, d, q, qbar);
```

```
end
```

```
endmodule
```

 

T FLIP FLOP :-

```
module t_ff(
```

```
    input t,rst,clk,
```

```
    output reg q,q_bar);
```

```
always@ (posedge clk) begin
```

```
    if(rst)begin
```

```
        q<=0;
```

```
        q_bar=1;
```

```
    end
```

```
    else begin
```

```
        if(t)begin
```

```

        q<=0;

        q_bar<=1;

    end

    else begin

        q<=1;

        q_bar<=0;

    end

end

end

end

endmodule


module t_tb();

    reg t, rst, clk;

    wire q, q_bar;

    // Change port order based on your t_ff module

    t_ff dut(.clk(clk), .rst(rst), .t(t), .q(q), .q_bar(q_bar));

    // Clock generation

    initial clk = 0;

```

```
always #5 clk = ~clk;
```

```
initial begin
```

```
    rst = 1; t = 0; #15;
```

```
    rst = 0; #10;
```

```
    t = 0; #50;
```

```
    t = 1; #50;
```

```
    t = 0; #10;
```

```
    t = 1; #10;
```


```
    t = 0; #10;
```

```
    t = 1; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

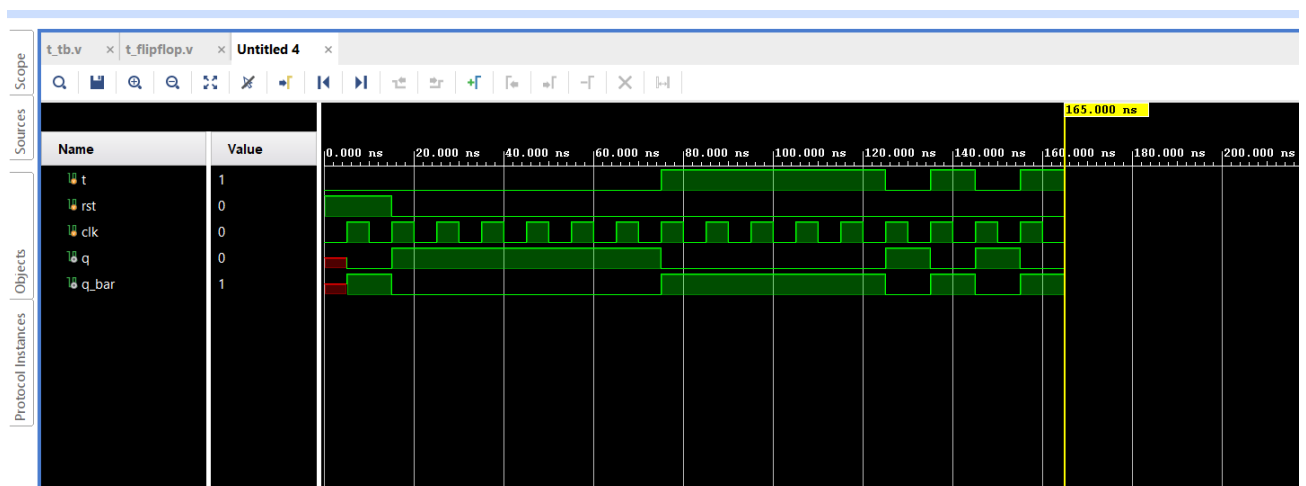

5. Universal Counter


AIM: Implement the Universal Counter.

Tools: Xilinx Vivado HLx Editions 2018.2 - Z7 FPGA Board (xc7z010clg400-1)

Theory:

Universal Counter:

- These types of counters fall under the category of synchronous controller counter.
- Here the mode control input is used to decide whether which sequence will be generated by the counter.
- In this case, mode control input is used to decide whether the counter will perform up counting or down counting.
- Designing of such a counter is the same as designing a synchronous counter but the extra combinational logic for mode control input is required.

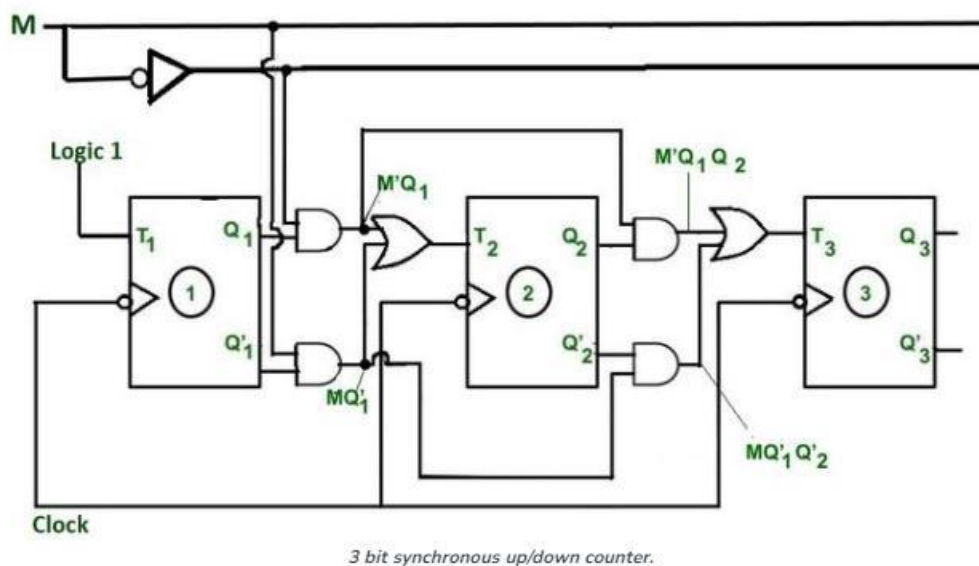

Code:-

```
module synchronous_counter #(parameter SIZE=4)(  
  
    input clk, rst_n, up,  
  
    output reg [SIZE-1:0] cnt );  
  
    always @(posedge clk)  
  
        if (!rst_n) cnt <= 0;  
  
        else cnt <= up ? cnt + 1 : cnt - 1;  
  
endmodule  
  
module tb;  
  
    reg clk = 0, rst_n = 0, up = 1;  
  
    wire [3:0] cnt;  
  
    synchronous_counter uut (.clk(clk), .rst_n(rst_n), .up(up), .cnt(cnt));  
  
    always #2 clk = ~clk;  
  
    initial begin  
  
        #4 rst_n = 1;  
  
        #80 rst_n = 0;  
  
        #4 rst_n = 1; up = 0;  
  
        #50 $finish;  
  
    end  
  
endmodule
```



 

6. SRAM Design

AIM: Implement the SRAM Memory.

Tools: Xilinx Vivado HLx Editions 2018.2 - Z7 FPGA Board (xc7z010clg400-1)

Theory:

Random Access Memory is the temporary memory used in a processor or the digital system which requires larger memory for storing temporary data. When designing any system on FPGA, sometimes we require a RAM block which is also called BRAM or block RAM. In this post, we'll how to describe a RAM in Verilog HDL. Most of the latest FPGAs have BRAM and if we synthesize this, it will be synthesized into a BRAM



Code:-

```
module memory_32b_8gb #(parameter dw=32, parameter aw=31)(
    input clk, cs, wen,
    input [dw-1:0] data_in,
    input [aw-1:0] addr,
    output reg [dw-1:0] data_out
);
```

```
reg [dw-1:0] mem[0:(1<<aw)-1];
```

```
always @(posedge clk) begin
```

```
    if (cs & wen) begin
```

```
        mem[addr] <= data_in;
```

```
    end
```

```
end
```

```
always @(posedge clk) begin
```

```
    if (cs & ~wen) begin
```

```
        data_out <= mem[addr];
```

```
    end
```

```
end
```

```
endmodule
```

```
module tb_memory_32b_8gb();
```

```
    reg clk, cs, wen;
```

```
    reg [31:0] data_in;
```

```
    reg [30:0] addr;
```

```
    wire [31:0] data_out;
```

```
    memory_32b_8gb #(.dw(32), .aw(31)) dut (
```

```
        .clk(clk),
```

```
        .cs(cs),
```

```
.wen(wen),  
  
.data_in(data_in),  
  
.addr(addr),  
  
.data_out(data_out)  
  
);  
  
always #5 clk = ~clk;
```

```
initial begin
```

```
    clk = 0;
```

```
end
```

```
initial
```

```
begin
```

```
    cs = 1;
```

```
    wen = 0;
```

```
    addr = 0;
```

```
    #10;
```

```
    wen = 1;
```

```
    data_in = 32'hA5A5A5A5; addr = 28'h0;
```

```
    #10;
```

```
    data_in = 32'hB6B6B6B6; addr = 28'h1;
```

```
    #10;
```

```
data_in = 32'hC7C7C7C7; addr = 28'h2;
```

```
#10;
```

```
data_in = 32'hD8D8D8D8; addr = 28'h3;
```

```
#10;
```

```
data_in = 32'hE9E9E9E9; addr = 28'h4;
```

```
#10;
```

```
wen = 0;
```

```
addr = 28'h0;
```

```
#10;
```

```
$display("Data at address 0: %h", data_out);
```

```
addr = 28'h1;
```

```
#10;
```

```
$display("Data at address 1: %h", data_out);
```

```
addr = 28'h2;
```

```
#10;
```

```
$display("Data at address 2: %h", data_out);
```

```
addr = 28'h3;
```

```
#10;
```

```
$display("Data at address 3: %h", data_out);
```

```
addr = 28'h4;
```


```
#10;
```

```
$display("Data at address 4: %h", data_out);
```

```
$finish();
```

```
end
```

```
endmodule
```

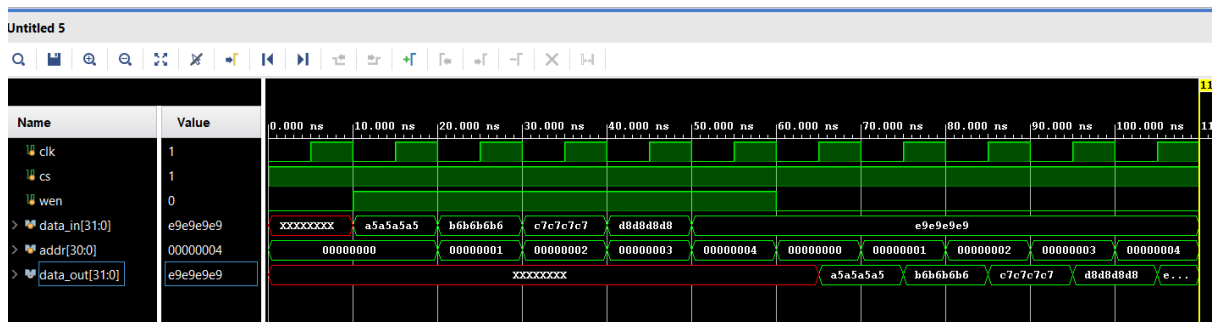

7. Universal Shift Register

AIM: Implement the Universal Shift Registers.

Tools: Xilinx Vivado HLx Editions 2018.2 - Z7 FPGA Board (xc7z010clg400-1)

Theory:

- When we have bi directional and parallel loading then that register is known as Universal shift register.
- We are using 4x1 mux and 2 select line's are connected to all 4 registers.
- The universal shift register can store the data in parallel and can transmit the data in parallel.
- In the same manner the data can stored and transmitted by serial path through shift left and shift right operations.

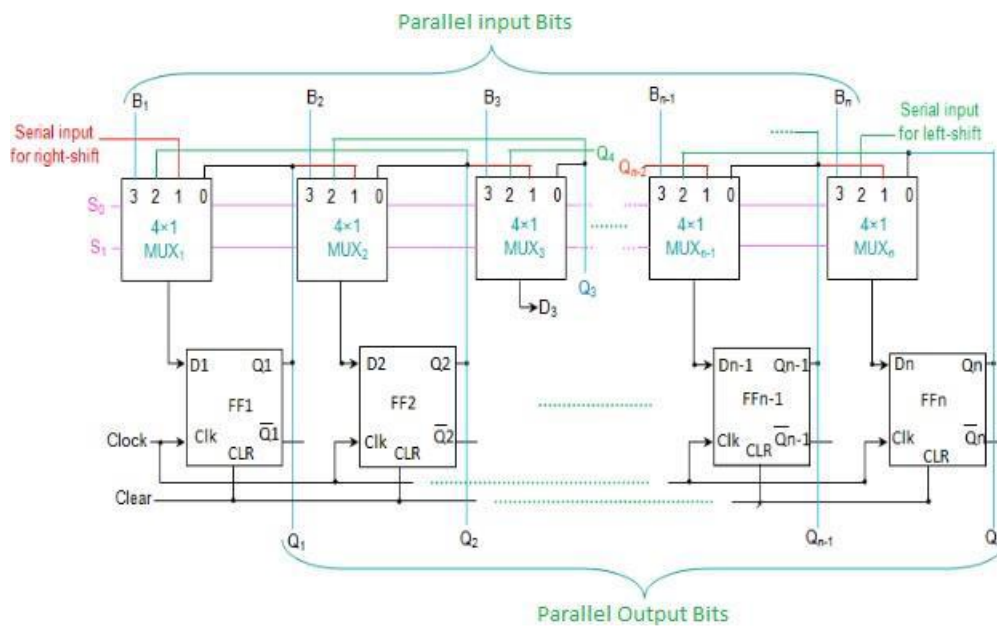


Table:-

S0	S1	Operating Mode
0	0	Locked
1	0	Shift-Right
0	1	Shift-Left
1	1	Parallel Loading

OPERATION:

When $S_0 = 0$ and $S_1 = 0$, then the universal shift register will be in locked state, that means no operation will be performed.

When $S_0 = 1$ and $S_1 = 0$, then it will shift the data to right, that is shift right operation is performed.

When $S_0 = 0$ and $S_1 = 1$, then it will shift the data to right, that is shift left operation is performed.

When $S_0 = 0$ and $S_1 = 0$, then the register results in PARALLEL LOAD operation.

Code:-

```
module universal #(
    parameter WIDTH = 4
)(
    output reg [WIDTH-1:0] q,
    input          clk,
    input          rst,    // Active-high synchronous reset
    input  [1:0]   s,      // 00: hold, 01: shift right, 10: shift left, 11: load
    input [WIDTH-1:0] din
);

always @(posedge clk) begin
    if (rst) begin
        q <= {WIDTH{1'b0}};
    end else begin
        case (s)
```



```

2'b00: q <= q;           // Hold

2'b01: q <= {1'b0, q[WIDTH-1:1]}; // Shift right (zero-fill)

2'b10: q <= {q[WIDTH-2:0], 1'b0}; // Shift left (zero-fill)

2'b11: q <= din;         // Parallel load

default: q <= q;

endcase

end

end

endmodule

module universal_tb;

reg clk = 0, rst = 1;

reg [1:0] s;

reg [3:0] din;

wire [3:0] q;

universal dut (.q(q), .clk(clk), .rst(rst), .s(s), .din(din));

always #5 clk = ~clk; // 10 ns clock period

initial begin

$monitor("t=%0t | rst=%b s=%b din=%b q=%b", $time, rst, s, din, q);

```

```
// Reset for 10 ns
```

```
#10 rst = 0;
```

```
// Stimulus sequence using delays
```

```
#10 s = 2'b11; din = 4'b1100; // Load
```

```
#10 s = 2'b00;           // Hold
```

```
#10 s = 2'b01;           // Shift right
```

```
#10 s = 2'b10;           // Shift left
```

```
#10 s = 2'b11; din = 4'b1010; // Load again
```


```
#10 s = 2'b00;           // Hold
```

```
#20 $finish;
```

```
end
```

```
endmodule
```

Result:

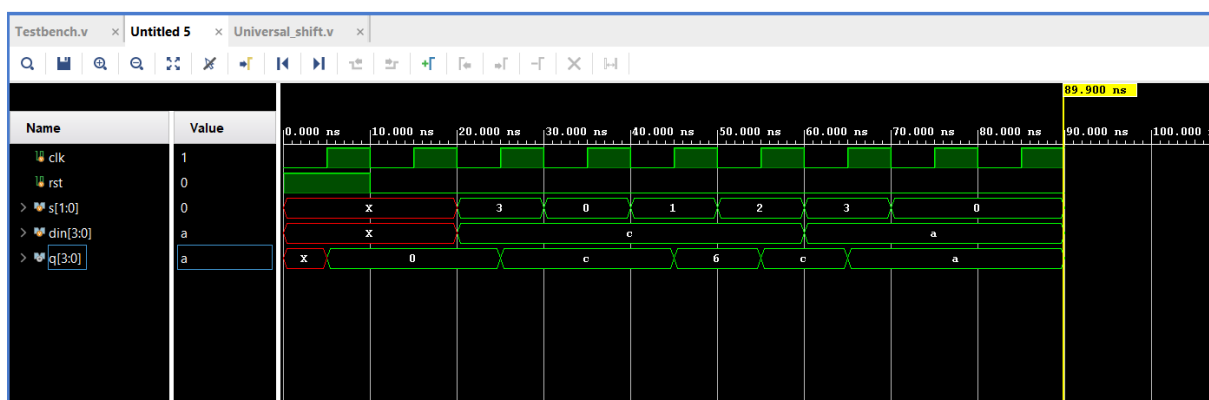

8. Floating Point Adder

AIM: Implement the Floating Point Adder.

Tools: Xilinx Vivado HLx Editions 2018.2 - Z7 FPGA Board (xc7z010clg400-1)

Theory:


- Lets take an example of binary addition: $23.5 + 452.752 = 476.252$
 - To add 23.5 and 452.752 in IEEE 754 format, the steps involve
 - converting the numbers into their IEEE 754 representation,
 - aligning the exponents,
 - performing the addition,
 - and normalizing the result.

Step	Description	23.5	452.752
1	Convert to Binary	10111.1	111000100.1100001111010111
2	Normalize	1.01111×2^4	$1.110001001100001111010111 \times 2^8$
3	Calculate Exponent (with bias)	$4 + 127 = 131$, Binary: 10000011	$8 + 127 = 135$, Binary: 10000111
4	Mantissa (drop leading 1, 23 bits)	011110000000000000000000	11000100110000111101011
5	IEEE 754 Representation	0 10000011 011110000000000000000000	0 10000111 11000100110000111101011
6	Align Exponents (shift smaller mantissa to match larger exponent)	Mantissa shifted: 0.000101111×2^8	Mantissa stays: $1.11000100110000111101011 \times 2^8$
7	Add Mantissas	Add: $0.000101111 + 1.11000100110000111101011 \rightarrow 1.11011100010000111101011$	

8	Normalize the Result	Already normalized: $1.11011100010000111101011 \times 2^8$	
9	Construct Final IEEE 754 Representation	Sign: 0, Exponent: 135, Mantissa: 11011100010000111101011	
10	Final IEEE 754 Binary Representation	0 10000111 11011100010000111101011	
11	Convert Back to Decimal	476.252	

Final Answer:

$$23.5 + 452.752 = 476.252$$

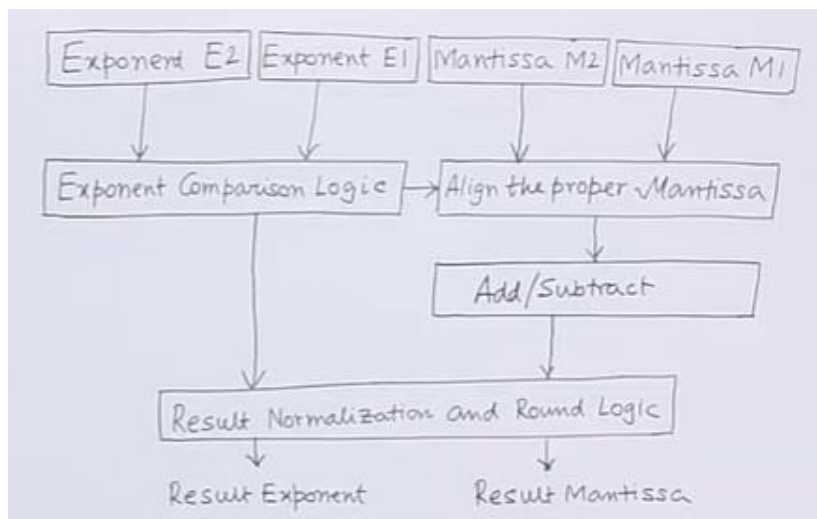

Code:-

```
`timescale 1ns / 1ps
```

```
module single_precision_add (
    input [31:0] a, // Input IEEE 754 number 1
    input [31:0] b, // Input IEEE 754 number 2
    output [31:0] result // Output IEEE 754 result
);
```

```
// Internal Signals
```

```
reg sign_a, sign_b, sign_res;
```

```
reg [7:0] exp_a, exp_b, exp_res, exp_sum;
```

```
reg [23:0] mant_a, mant_b, mant_res;
```

```
reg [24:0] mant_sum;
```

```
reg [7:0] exp_diff;
```

```
reg [7:0] exp_temp;
```

```
reg [23:0] mant_shifted;
```

```
// Step 1: Split Inputs into Sign, Exponent, and Mantissa
```

```
always @(*)
```

```
begin : SPLIT_INPUTS
```

```
    sign_a = a[31];
```

```
    sign_b = b[31];
```

```
    exp_a = a[30:23];
```

```
    exp_b = b[30:23];
```

```
    mant_a = {1'b1, a[22:0]}; // Add implicit leading 1
```

```
    mant_b = {1'b1, b[22:0]};
```

```
end
```

```
// Step 2: Align Exponents
```

```
always @(*)
```

```
begin : ALIGN_EXPONENTS
```

```
    if (exp_a > exp_b)
```

```
    begin
```

```
        exp_diff = exp_a - exp_b;
```

```
        exp_sum = exp_a;
```

```

        mant_shifted = mant_b >> exp_diff;

        mant_sum = mant_a + mant_shifted;

    end

    else

    begin

        exp_diff = exp_b - exp_a;

        exp_sum = exp_b;

        mant_shifted = mant_a >> exp_diff;

        mant_sum = mant_b + mant_shifted;

    end

end

// Step 3: Normalize Result

always @(*)

begin : NORMALIZE

    if (mant_sum[24])

    begin

        mant_res = mant_sum[24:1]; // Normalize mantissa

        exp_res = exp_sum + 1; // Adjust exponent

    end

    else

    begin

        mant_res = mant_sum[23:0];

        exp_res = exp_sum;

    end

end

end

```

```

// Step 4: Combine Sign, Exponent, and Mantissa

```

```
    assign result = {sign_a, exp_res, mant_res[22:0]};
```

```
endmodule
```

```
//Testbench
```

```
`timescale 1ns / 1ps
```

```
module single_precision_add_tb;
```

```
    // Inputs
```

```
    reg [31:0] a;
```

```
    reg [31:0] b;
```

```
    real real_a;
```

```
    real real_b;
```

```
    // Output
```

```
    wire [31:0] result;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    single_precision_add uut (
```

```
        .a(a),
```

```
        .b(b),
```

```
        .result(result)
```

```
    );
```

```
    // Task to display IEEE 754 output
```

```

task display_result;

    input [31:0] res;

    begin

        $display("Result (Binary) = %b", res);

        $display("Result (Hex)  = %h", res);

        #10;

    end

endtask


// Testbench Procedure

initial

begin : TEST_CASES

    $display("\n--- Test Case 1: 23.5 + 452.752 ---");

    real_a = 23.5;

    real_b = 452.752;

    a = $realtobits(real_a);

    b = $realtobits(real_b);

    #10;

    display_result(result);

    $display("\n--- Test Case 2: 12.75 + 6.125 ---");

    real_a = 12.75;

    real_b = 6.125;

    a = $realtobits(real_a);

    b = $realtobits(real_b);

    #10;

    display_result(result);


    $display("\n--- Test Case 3: -15.25 + 31.5 ---");

```



```

real_a = -15.25;

real_b = 31.5;

a = $realtobits(real_a);

b = $realtobits(real_b);

#10;

display_result(result);

$display("\n--- Test Case 4: 7.75 + -3.625 ---");

real_a = 7.75;

real_b = -3.625;

a = $realtobits(real_a);

b = $realtobits(real_b);

#10;

display_result(result);


$stop;

end

```

endmodule

Result:-

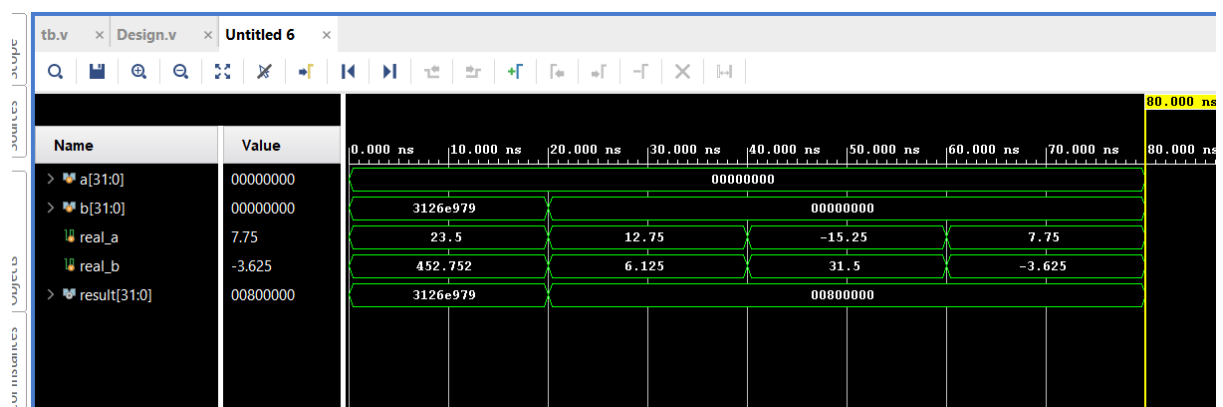

9. Floating Point Multiplier

AIM: Implement the Floating Point Multiplier.

Tools: Xilinx Vivado HLx Editions 2018.2 - Z7 FPGA Board (xc7z010clg400-1)

Theory:

Lets take an example of binary Multiplication: $23.5 \times 452.72 = 10655.192$

To multiply 23.5 and 452.752 in IEEE 754 single-precision format, the steps involve:

1. Converting the numbers into their IEEE 754 representations
2. Adding the exponents
3. Multiplying the mantissas
4. Normalizing the result
5. Constructing the final IEEE 754 representation

Step 1: Convert the Numbers to Binary and Normalize

For 23.5:

1. Convert 23.5 to binary: 10111.1.
2. Normalize: 1.01111×2^4 .
3. Exponent: Add the bias 127: $4 + 127 = 131 \rightarrow 10000011$ in binary.
4. Mantissa: Drop the leading 1 $\rightarrow 0111100000000000000000$ (23 bits).
 - Final IEEE 754 (32-bit): 0 10000011 0111100000000000000000.

For 452.752:

1. Convert 452.752 to binary: 111000100.1100001111010111.
2. Normalize: $1.11000100110000111101011 \times 2^8$.
3. Exponent: Add the bias 127: $8 + 127 = 135 \rightarrow 10000111$ in binary.
4. Mantissa: Drop the leading 1 $\rightarrow 11000100110000111101011$ (23 bits).
 - Final IEEE 754 (32-bit): 0 10000111 11000100110000111101011.

Step 2: Add the Exponents

1. Exponent of 23.5 = 131, Exponent of 452.752 = 135.
2. Add the exponents and subtract the bias:
$$131 + 135 - 127 = 139$$
3. New Exponent: 139, Binary: 10001011.

Step 3: Multiply the Mantissas

1. Mantissa of 23.5 (with implicit 1): 1.01111.
2. Mantissa of 452.752 (with implicit 1): 1.1100010011.
3. Multiply the mantissas:
$$1.01111 \times 1.1100010011 = 1.10100101111 \text{ (approx)}$$

The result is already normalized.

Step 4: Assemble the Final IEEE 754 Format

1. Sign bit: 0 (since the result is positive).
2. Exponent: 139, Binary: 10001011.
3. Mantissa: Keep the first 23 bits after the leading 1:

10100101111000000000000

Final IEEE 754 Representation (32-bit):

0 10001011 10100101111000000000000

Step 5: Convert Back to Decimal

1. The result in binary: $1.10100101111 \times 2^{12}$.
2. Convert to decimal:
$$1.10100101111 \times 2^{12} = 10655.192$$

Final Answer:

$$23.5 \times 452.752 = 10655.192$$

- IEEE 754 Single-Precision Representation (Binary):
0 10001011 10100101111000000000000
- Hexadecimal: 45.498000.

Code:-

```
`timescale 1ns / 1ps
```

```
module single_precision_mult (  
  
    input [31:0] a, // Input IEEE 754 number 1  
  
    input [31:0] b, // Input IEEE 754 number 2  
  
    output [31:0] result // Output IEEE 754 result  
  
);
```

```

// Internal Signals

reg sign_a, sign_b, sign_res;

reg [7:0] exp_a, exp_b, exp_res;

reg [23:0] mant_a, mant_b;

reg [47:0] mant_mult;

reg [7:0] exp_sum;

reg [22:0] mant_res;

// Step 1: Split Inputs into Sign, Exponent, and Mantissa

always @(*)

begin : SPLIT_INPUTS

    sign_a = a[31];

    sign_b = b[31];

    exp_a = a[30:23];

    exp_b = b[30:23];

    mant_a = {1'b1, a[22:0]}; // Add implicit leading 1

    mant_b = {1'b1, b[22:0]};

end

// Step 2: Calculate Sign and Exponent

always @(*)

begin : CALCULATE_SIGN_EXP

    sign_res = sign_a ^ sign_b; // XOR of signs for result sign

```

```

        exp_sum = exp_a + exp_b - 127; // Add exponents and subtract bias

    end

// Step 3: Multiply Mantissas

    always @(*)

    begin : MULTIPLY_MANTISSAS

        mant_mult = mant_a * mant_b; // Multiply mantissas

    end

// Step 4: Normalize Result

    always @(*)

    begin : NORMALIZE

        if (mant_mult[47])

            begin

                mant_res = mant_mult[46:24]; // Normalize mantissa (shift right by 1)

                exp_res = exp_sum + 1; // Adjust exponent

            end

        else

            begin

                mant_res = mant_mult[45:23]; // Use result directly

                exp_res = exp_sum;

            end

        end

    end

end

```

```
// Step 5: Combine Sign, Exponent, and Mantissa
```

```
assign result = {sign_res, exp_res, mant_res};
```

```
endmodule
```

```
//Testbench
```

```
`timescale 1ns / 1ps
```

```
module single_precision_mult_tb;
```

```
    // Inputs
```

```
    reg [31:0] a;
```

```
    reg [31:0] b;
```

```
    real real_a;
```

```
    real real_b;
```

```
    // Output
```

```
    wire [31:0] result;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    single_precision_mult uut (
```

```
        .a(a),
```

```
        .b(b),
```

```
        .result(result)
```

```
    );
```

```
    // Task to display IEEE 754 output
```

```
    task display_result;
```

```

input [31:0] res;

begin

    $display("Result (Binary) = %b", res);

    $display("Result (Hex)  = %h", res);

    #10;

end

endtask


// Testbench Procedure

initial

begin : TEST_CASES

    $display("\n--- Test Case 1: 23.5 * 452.752 ---");

    real_a = 23.5;

    real_b = 452.752;

    a = $realtobits(real_a);

    b = $realtobits(real_b);

    #10;

    display_result(result);

    $display("\n--- Test Case 2: 12.75 * 6.125 ---");

    real_a = 12.75;

    real_b = 6.125;

```

```

a = $realtobits(real_a);

b = $realtobits(real_b);

#10;

display_result(result);

$display("\n--- Test Case 3: -15.25 * 31.5 ---");

real_a = -15.25;

real_b = 31.5;

a = $realtobits(real_a);

b = $realtobits(real_b);

#10;

display_result(result);

$display("\n--- Test Case 4: 7.75 * -3.625 ---");

real_a = 7.75;

real_b = -3.625;

a = $realtobits(real_a);

b = $realtobits(real_b);

#10;

display_result(result);

$stop;

```

```

end


```

```

endmodule

```


Results:-

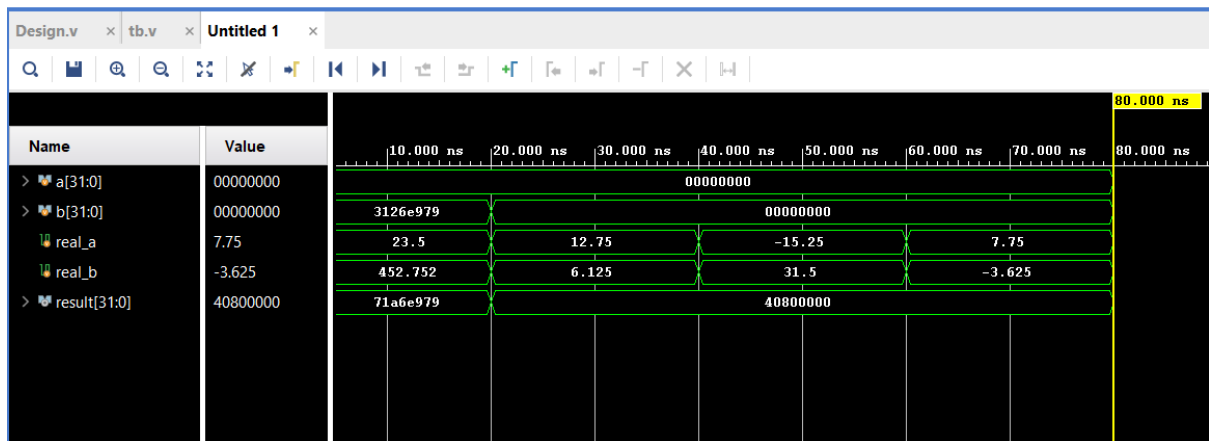

10. Boot Multiplier

AIM: Implement the Boot Multiplier.

Tools: Xilinx Vivado HLx Editions 2018.2 - Z7 FPGA Board (xc7z010clg400-1)

Theory:

Booth's Multiplier

In Booth's multiplier works on Booth's Algorithm that does the multiplication of 2's complement notation of two signed binary numbers.

Flow chart of Booth's Algorithm

Please note of below abbreviations used:

A – holds Multiplicand

B – holds Multiplier


Q = B

Q0 – holds 0th bit (LSB) of Q register

Q-1 – 1-bit variable/register.

Acc – Accumulator holds the result of intermediate addition/subtraction.

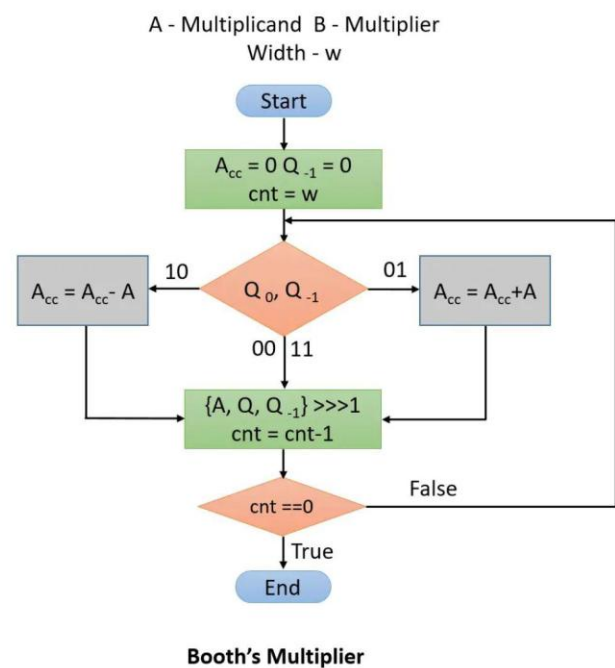Count = max(width of multiplicand register, width of multiplier register)



Code:-

```
`timescale 1ns / 1ps
```

```
module booth_multiplier (
```

```
    input [3:0] multiplicand, // 4-bit multiplicand (M)
```



```

reg [3:0] M;          // Multiplicand

reg [2:0] n;          // Counter for bits

// Determine sign and magnitude of the product

assign sign = product[7];

assign magnitude = sign ? (~product + 8'd1) : product;

// State transition logic

always @(posedge clk)

begin

    if (rst)

        current_state <= INIT;

    else

        current_state <= next_state;

end

// Next state logic

always @(*)

begin

    next_state = current_state;

    case (current_state)

        INIT:      next_state = DECISION;

        DECISION:  case ({Q[0], q_0})

                        2'b01: next_state = ADD;

```

```

        2'b10: next_state = SUB;

        default: next_state = SHIFT_RIGHT;

    endcase

    ADD:      next_state = SHIFT_RIGHT;

    SUB:      next_state = SHIFT_RIGHT;

    SHIFT_RIGHT:  next_state = DEC_COUNTER;

    DEC_COUNTER:  next_state = CHECK_DONE;

    CHECK_DONE:   next_state = (n == 0) ? RESULT_EXTRACT : DECISION;

    RESULT_EXTRACT: next_state = STOP;

    STOP:        next_state = STOP;

endcase

end

// State actions

always @(posedge clk)

begin

    if (rst)

    begin

        A <= 4'b0000;

        Q <= 4'b0000;

        q_0 <= 1'b0;

        M <= 4'b0000;

```

```

n <= 3'd4;

product <= 8'b00000000;

end

else

begin

    case (current_state)

        INIT: begin

            A <= 4'b0000;

            Q <= multiplier;

            q_0 <= 1'b0;

            M <= multiplicand;

            n <= 4;

        end

        ADD: begin

            A <= A + M; // Add multiplicand to accumulator

        end

        SUB: begin

            A <= A - M; // Subtract multiplicand from accumulator

        end

        SHIFT_RIGHT: begin

            q_0 <= Q[0];

```

```

        Q <= {A[0], Q[3:1]};

        A <= {A[3], A[3:1]}; // Arithmetic Shift Right

    end

    DEC_COUNTER: begin

        n <= n - 1;

    end

    RESULT_EXTRACT: begin

        product <= {A, Q}; // Combine A and Q

    end

    STOP: begin

        // Do nothing

    end

endcase

end

end

endmodule

Testbench:-

`timescale 1ns / 1ps

module booth_multiplier_tb1;

    // Testbench signals

    reg [3:0] multiplicand;

```

```
reg [3:0] multiplier;

reg clk;

reg rst;

wire [7:0] product;

wire sign;

wire [7:0] magnitude;

// Instantiate the DUT (Device Under Test)

booth_multiplier dut (

    .multiplicand(multiplicand),

    .multiplier(multiplier),

    .clk(clk),

    .rst(rst),

    .product(product),

    .sign(sign),

    .magnitude(magnitude)

);

// Clock generation

always #5 clk = ~clk;

// Task to print results

task print;

    input [3:0] in_multiplicand;
```



```

input [3:0] in_multiplier;

input [7:0] in_product;

input in_sign;

input [7:0] in_magnitude;

begin

    $display("Test Case: %d * %d, Product: %d, Sign: %b, Magnitude: %d",

        $signed(in_multiplicand), $signed(in_multiplier), $signed(in_product), in_sign,
in_magnitude);

    end

endtask

// Testbench logic

initial

begin

    // Initialize signals

    clk = 0;

    rst = 0;

    multiplicand = 0;

    multiplier = 0;

    // Apply reset

    rst = 1;

    #20;

    rst = 0;

```

```
// Test case: -7 x 3
```

```
multiplicand = 4'b1001; // -7 in 2's complement
```

```
multiplier = 4'b0011; // 3
```

```
#1000;
```

```
print(multiplicand, multiplier, product, sign, magnitude);
```

```
#10;
```

```
// Test case: -7 x 3
```

```
multiplicand = 4'b0001; // -7 in 2's complement
```

```
multiplier = 4'b0011; // 3
```

```
#1000;
```

```
print(multiplicand, multiplier, product, sign, magnitude);
```

```
#10;
```

```
$stop; // End simulation
```

```
end
```

```
endmodule
```

Output:-

